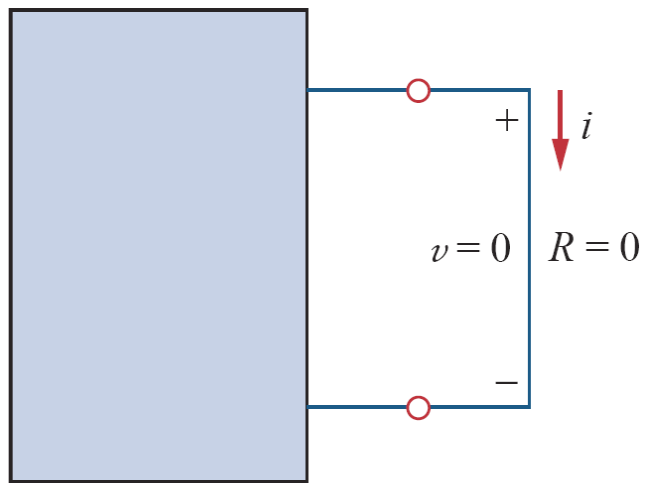


- Ohm's law states that the voltage  $v$  across a resistor is directly proportional to the current  $i$  flowing through

$$v = iR$$


The resistance  $R$  of an element denotes its ability to resist the flow of electric current; it is measured in ohms.

$$R = \frac{v}{i}$$




(a)

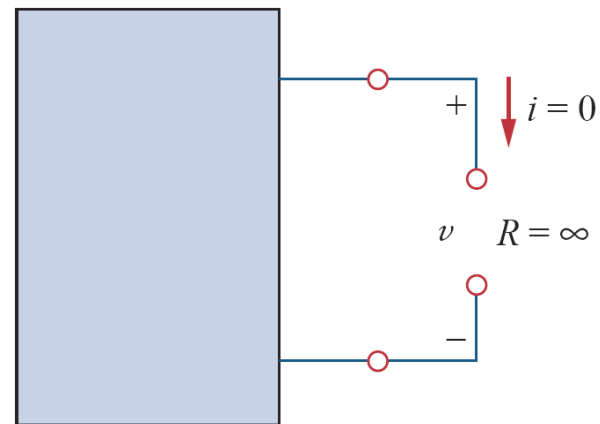A short circuit is a circuit element with resistance approaching zero.




(b)

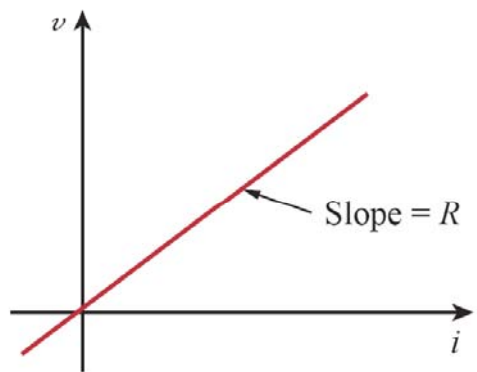An open circuit is a circuit element with resistance approaching infinity.



(a)

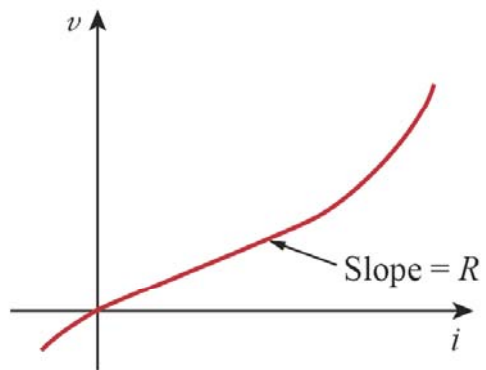


(b)

**Figure 2.7**

The  $i$ - $v$  characteristic of: (a) a linear resistor, (b) a nonlinear resistor.

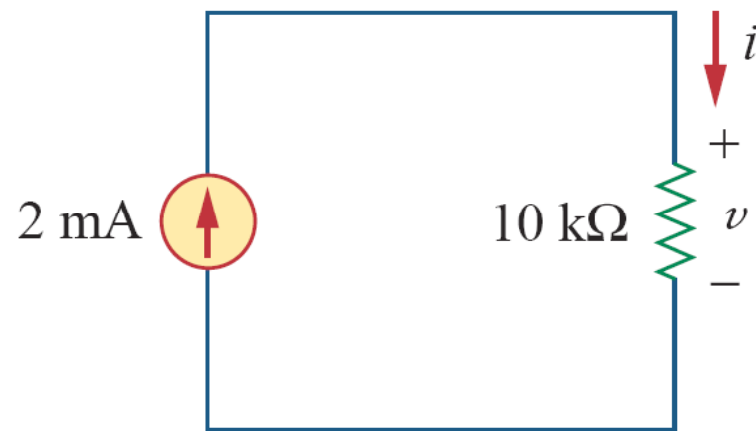
- Conductance is the ability of an element to conduct electric current; it is measured in mhos or siemens (S).



A branch represents a single element such as a voltage source or a resistor.


A node is the point of connection between two or more branches.

A loop is any closed path in a circuit.

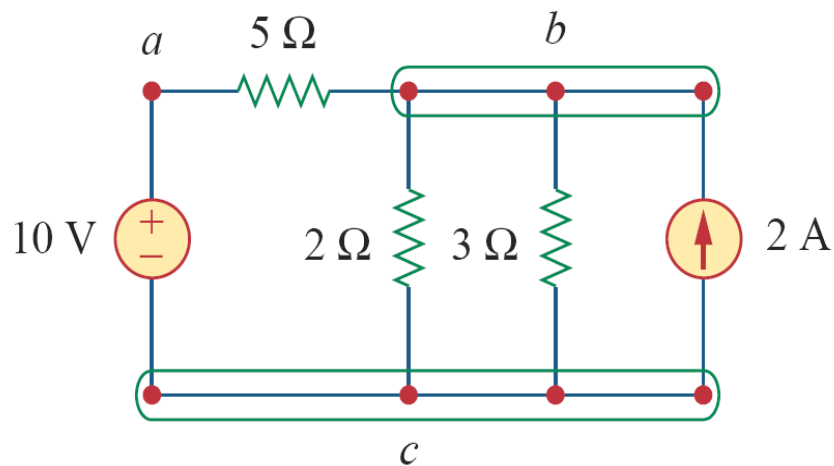

**Figure 2.10**

Nodes, branches, and loops.

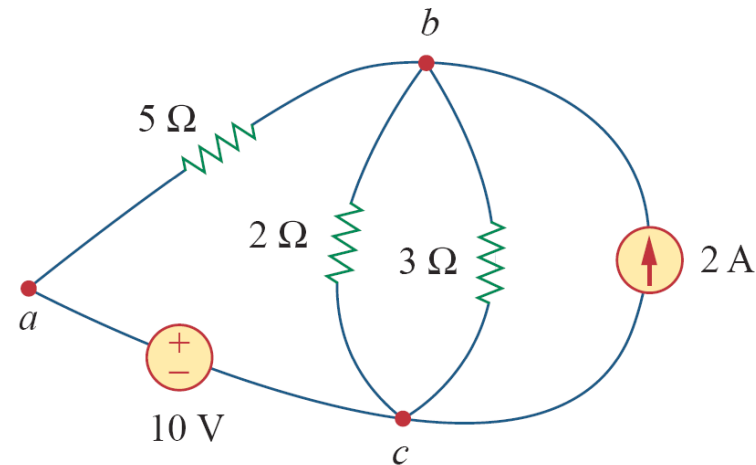

**Figure 2.11**


The three-node circuit of Fig. 2.10 is redrawn.

- Two or more elements are in series if they exclusively share a single node and consequently carry the same current.
- Two or more elements are in parallel if they are connected to the same two nodes and consequently have the same voltage across them.


# Kirchhoff's Laws

- Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node (or a closed boundary) is zero.

$$\sum_{n=1}^N i_n = 0$$

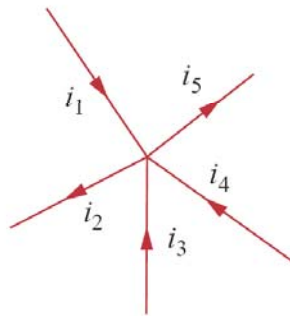


**Figure 2.16**  
Currents at a node illustrating KCL.

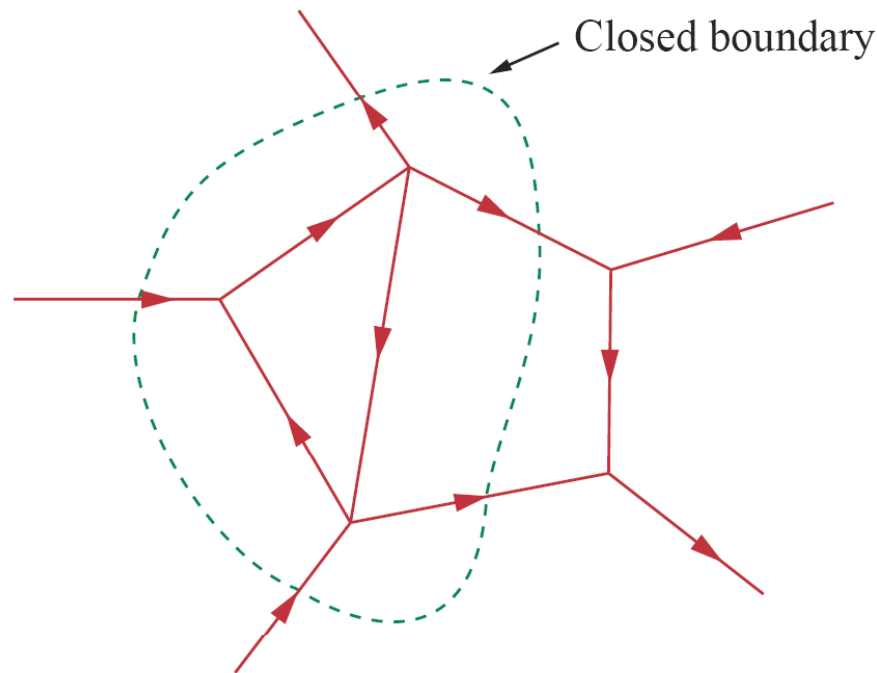

**Figure 2.17**  
Applying KCL to a closed boundary.


- Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

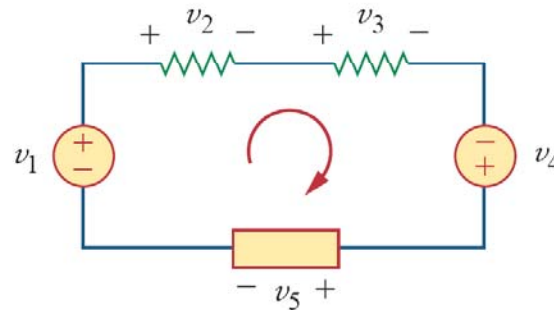

**Figure 2.19**


A single-loop circuit illustrating KVL.

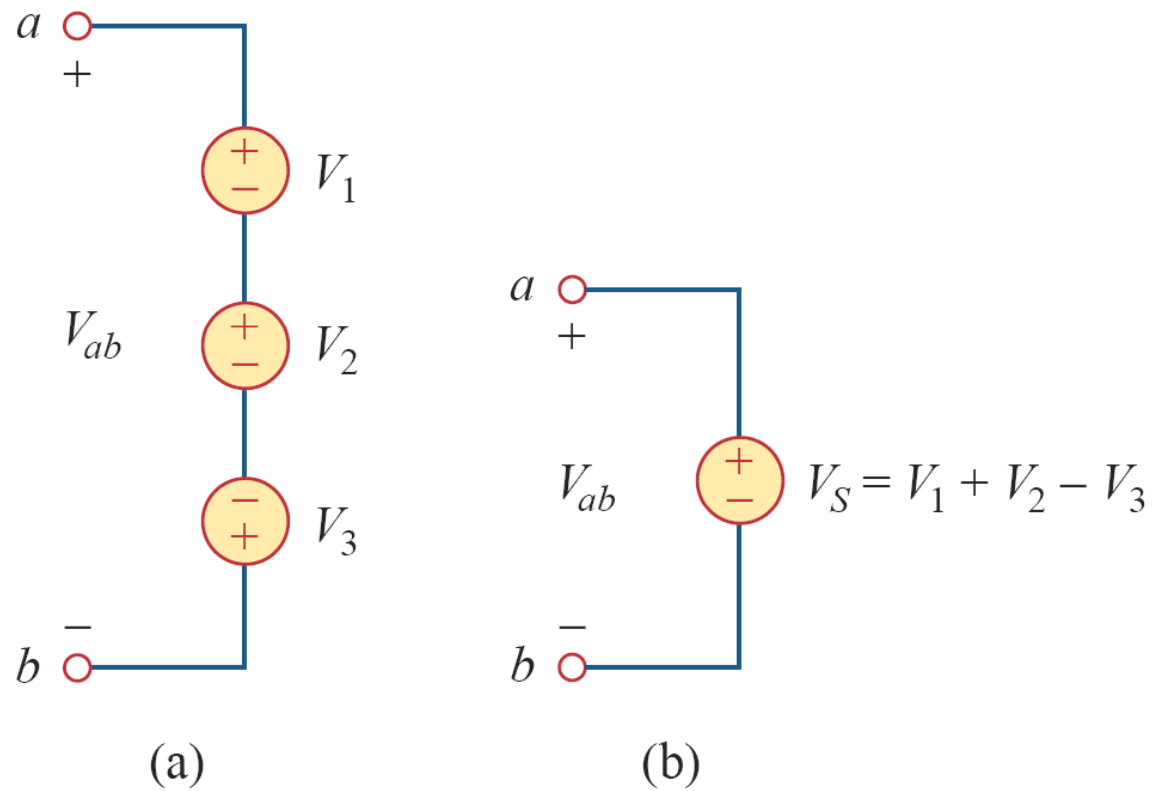


**Figure 2.20**

Voltage sources in series: (a) original circuit, (b) equivalent circuit.

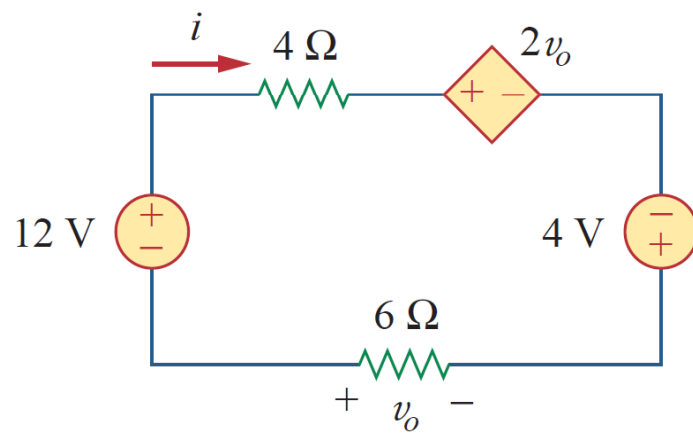Determine  $v_o$  and  $i$  in the circuit shown in Fig. 2.23(a).




(a)

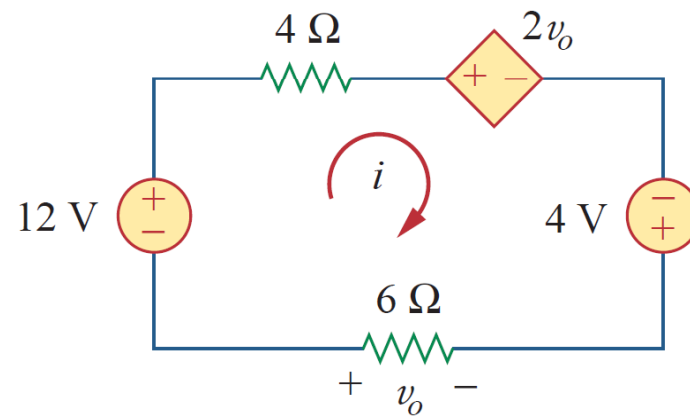


(b)

**Figure 2.23**


## Example 2.7

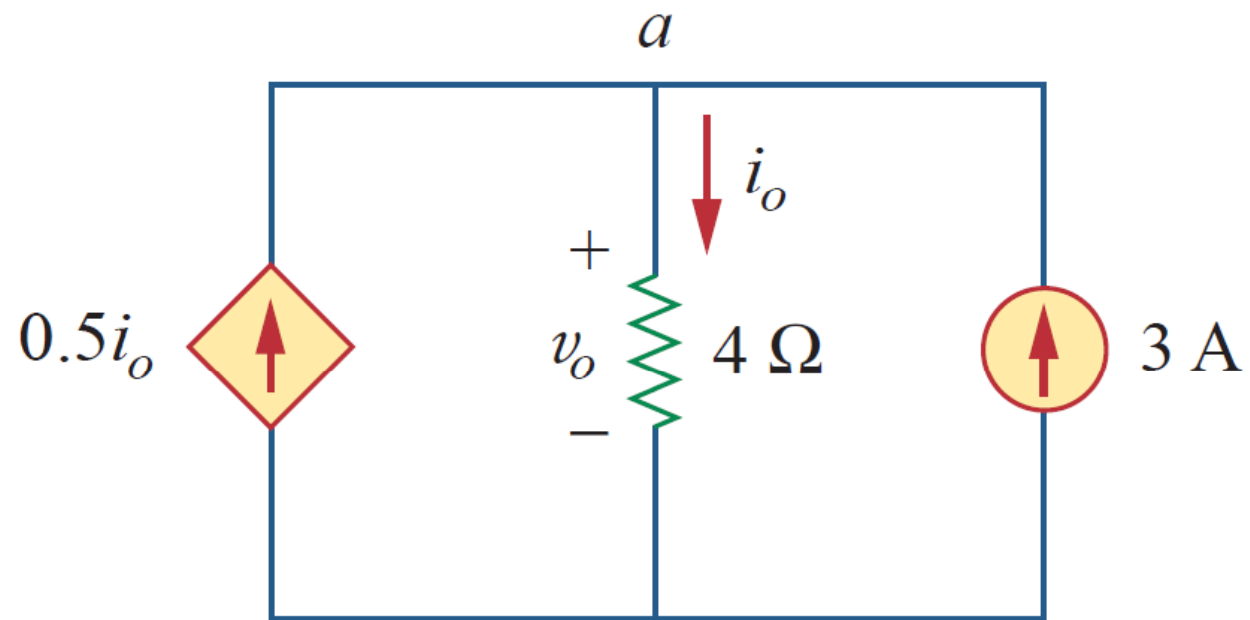

## Practice Problem 2.7

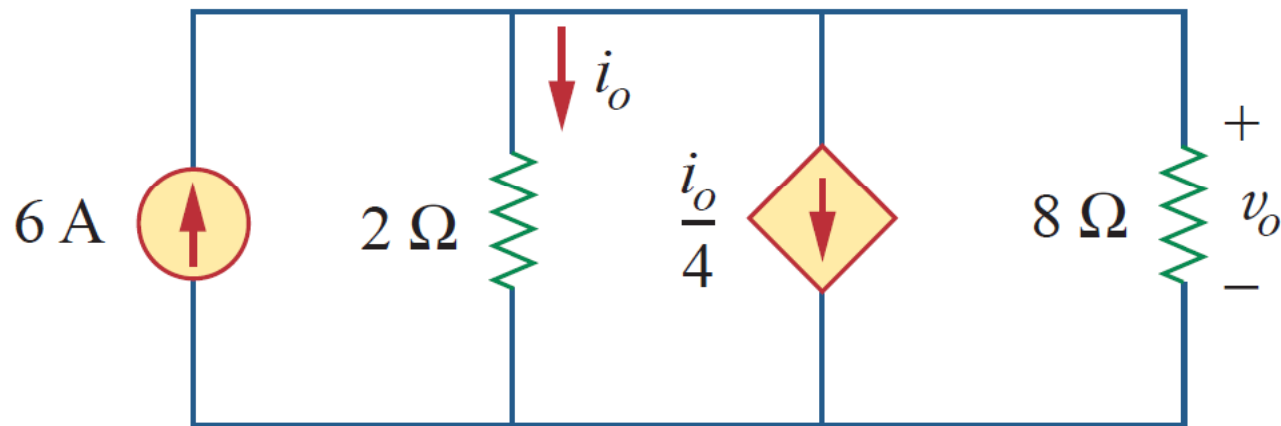


**Figure 2.26**

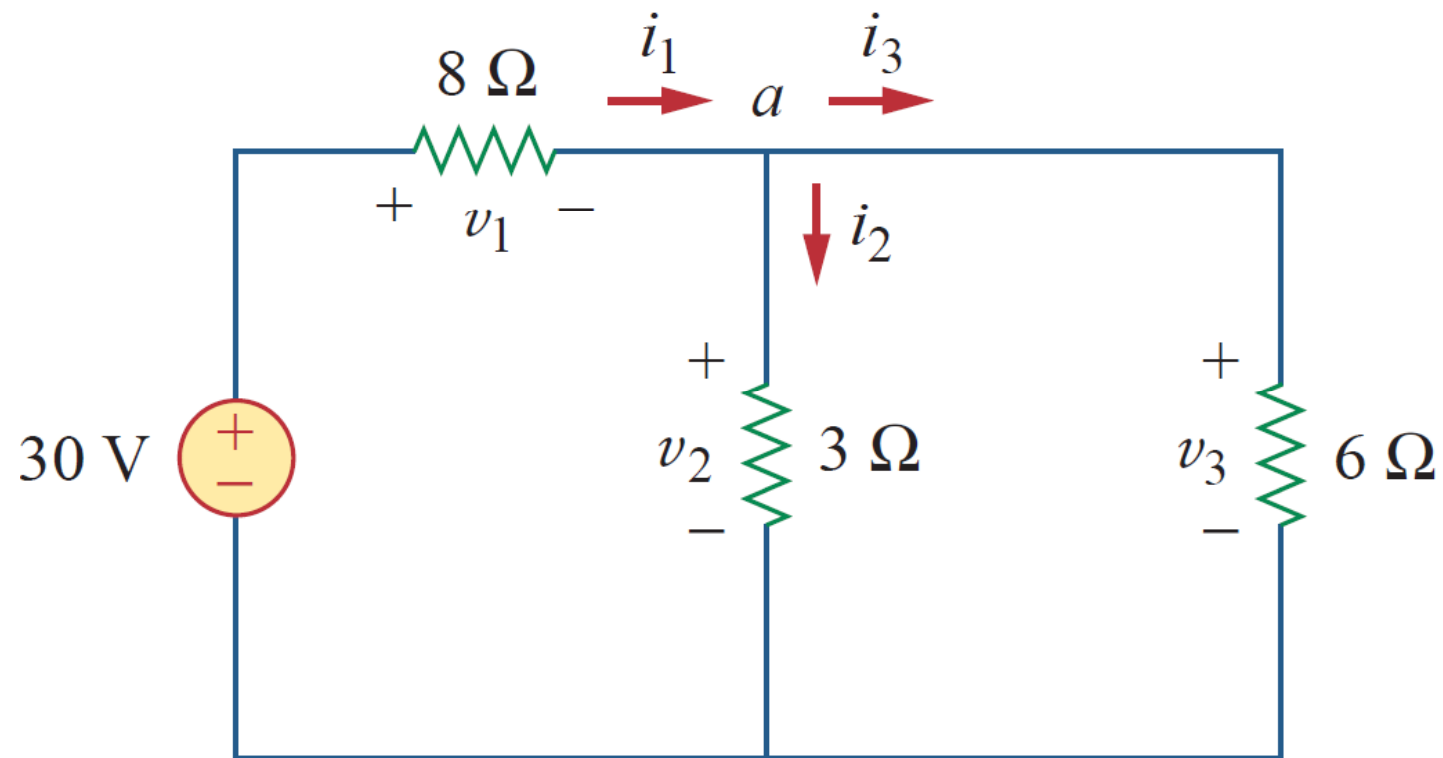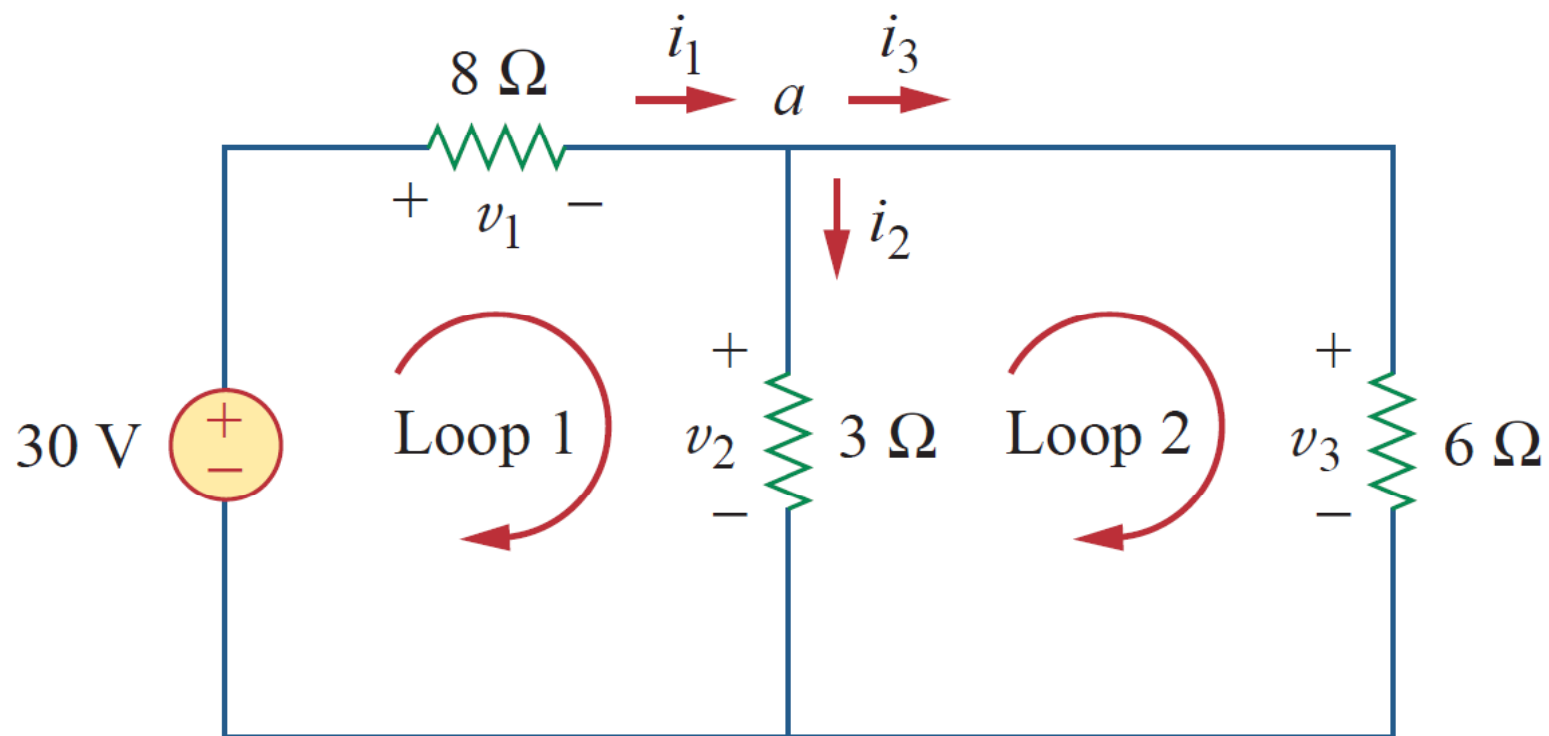


(a)

**Figure 2.27**



(b)

# Series Resistors and Voltage Division

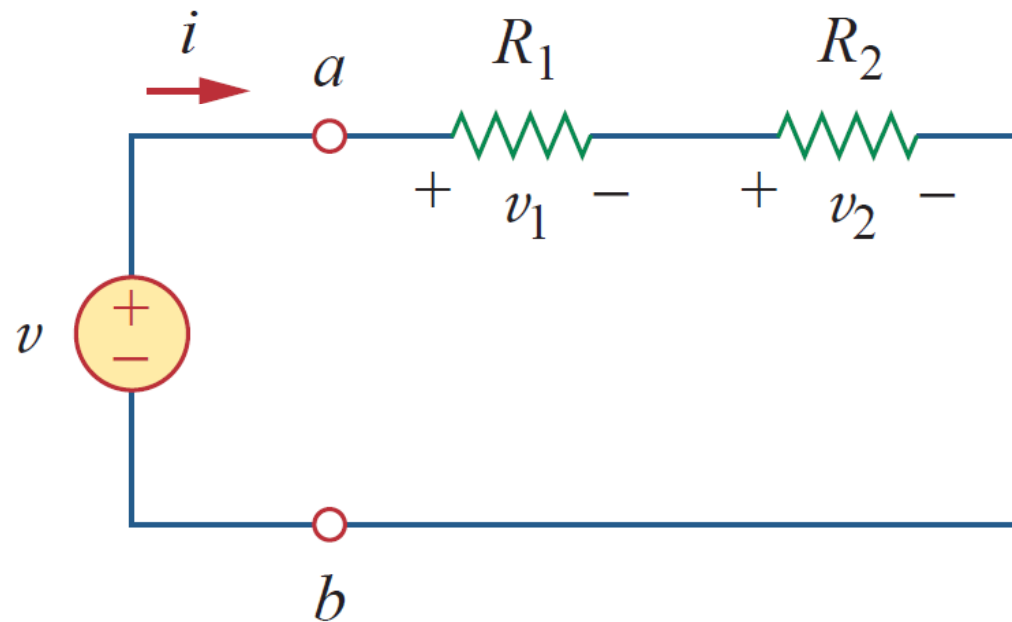

**Figure 2.29**

A single-loop circuit with two resistors in series.

The equivalent resistance of any number of resistors connected in series is the sum of the individual resistances.

For  $N$  resistors in series then,

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n \quad (2.30)$$

To determine the voltage across each resistor in Fig. 2.29, we substitute Eq. (2.26) into Eq. (2.24) and obtain


$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v \quad (2.31)$$

*principle of voltage division*

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$

# Parallel Resistors and Current Division

## Consider

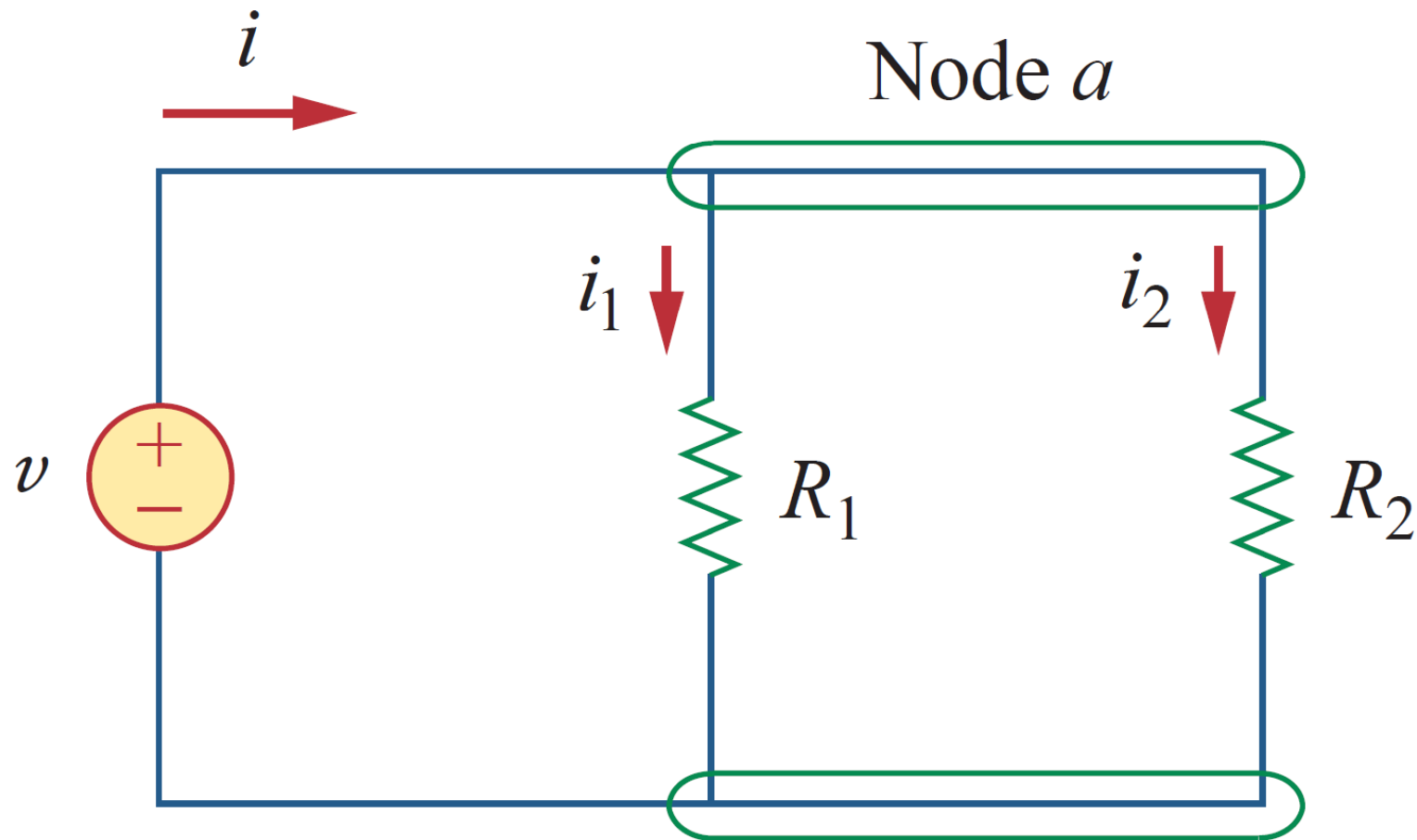

- The equivalent conductance of resistors connected in parallel is the sum of their individual conductances

$$G_{\text{eq}} = G_1 + G_2 + G_3 + \cdots + G_N \quad (2.40)$$

$$i_n = \frac{G_n}{G_1 + G_2 + \cdots + G_N} i$$